

IITB-RISC-23

EE309 COURSE PROJECT

ANUJA SATHE – 210070010

AYAN DAS- 210070016

BHAKTI MATSYAPAL - 210070021

DEBASISH PANDA – 21d070021

Contents

Overview of the project:	1
IITB-CPU Instruction Set Architecture.....	1
Design:.....	4
Instruction executions:.....	4
Control Variables:	9
Entities:.....	9
GITHUB Link.....	9

Overview of the project:

Designing a 6-stage pipelined processor, IITB-RISC-23, as per the ISA provided. IITB-RISC is a 16-bit very simple computer developed for the teaching that is based on the Little Computer Architecture. The IITB-RISC-23 is a 16-bit computer system with 8 registers. It follows the standard 6 stage pipelines (Instruction fetch, instruction decode, register read, execute, memory access, and write back). The architecture is optimized for performance, i.e., it includes hazard mitigation techniques which include feed-forwarding paths.

IITB-CPU Instruction Set Architecture

IITB-RISC is a 16-bit very simple computer developed for the teaching that is based on the Little Computer Architecture. The IITB-RISC-23 is an 8-register, 16-bit computer system. It has 8 general purpose registers (R0 to R7). Register R0 always stores Program Counter. All addresses are byte addresses and instructions. Always it fetches two bytes for instruction and data. This architecture uses condition code register which has two flags Carry flag (C) and Zero flag (Z). The IITB-RISC-23 is very simple, but it is general enough to solve complex problems. The architecture allows predicated instruction execution and multiple load and store execution. There are three machine-code instruction formats (R, I, and J type) and a total of 14 instructions.

R Type Instruction format

Opcode (4 bit)	Register A (RA) (3 bit)	Register B (RB) (3-bit)	Register C (RC) (3-bit)	Comple -ment (1 bit)	Condition (CZ) (2 bit)
-------------------	----------------------------	----------------------------	----------------------------	----------------------------	---------------------------

I Type Instruction format

Opcode (4 bit)	Register A (RA) (3 bit)	Register C (RC) (3-bit)	Immediate (6 bits signed)
-------------------	----------------------------	----------------------------	------------------------------

J Type Instruction format

Opcode (4 bit)	Register A (RA) (3 bit)	Immediate (9 bits signed)
-------------------	----------------------------	------------------------------

Instructions Encoding:

ADA:	00_01	RA	RB	RC	0	00
ADC:	00_01	RA	RB	RC	0	10
ADZ:	00_01	RA	RB	RC	0	01
AWC:	00_01	RA	RB	RC	0	11
ACA:	00_01	RA	RB	RC	1	00
ACC:	00_01	RA	RB	RC	1	10
ACZ:	00_01	RA	RB	RC	1	01
ACW:	00_01	RA	RB	RC	1	11
ADI:	00_00	RA	RB	6 bit Immediate		
NDU:	00_10	RA	RB	RC	0	00
NDC:	00_10	RA	RB	RC	0	10
NDZ:	00_10	RA	RB	RC	0	01
NCU:	00_10	RA	RB	RC	1	00

NCC:	00_10	RA	RB	RC	1	10
NCZ:	00_10	RA	RB	RC	1	01
LLI:	00_11	RA	9 bit Immediate			
LW:	01_00	RA	RB	6 bit Immediate		
SW:	01_01	RA	RB	6 bit Immediate		
LM:	01_10	RA	0 + 8 bits corresponding to Reg R0 to R7 (left to right)			
SM:	01_11	RA	0 + 8 bits corresponding to Reg R0 to R7 (left to right)			
BEQ:	10_00	RA	RB	6 bit Immediate		
BLT	10_01	RA	RB	6 bit Immediate		
BLE	10_01	RA	RB	6 bit Immediate		

JAL:	11_00	RA	9 bit Immediate offset	
JLR:	11_01	RA	RB	000_000
JRI	11_11	RA	9 bit Immediate offset	

Design:

Instruction executions:

1. ADA:

PC	→	MEM_ADDR, ALU2_A	ALU1:ADD
MEM1_DATA ₁₁₋₉	→	RF_A1	MEM1_RD=1
MEM1_DATA ₈₋₆	→	RF_A2	RF_RD=1
RF_D1	→	ALU1_A	RF_WR=1
ALU1_C	→	RF_D3	CMP=0
MEM1_DATA ₅₋₃	→	RF_A3	MEM2_RD=0
+2	→	ALU2_B	MEM2_WR=0
ALU2_C	→	PC	

2. ADC:

PC	→	MEM-	ALU1:ADD
1_ADDR, ALU2_A			MEM1_RD=1
if (C==1) : ADA			RF_RD=1
else :			RD_WR=1
+2	→	ALU2_B	CMP=0
ALU2_C	→	PC	MEM2_RD=0
			MEM2_WR=0

3. ADZ:

PC	→	MEM1_ADDR, ALU2_A	ALU1:ADD
if (Z==1) : ADA			MEM1_RD=1
else :			RF_RD=1
+2	→	ALU2_B	RD_WR=1
ALU2_C	→	PC	CMP=0
			MEM2_RD=0
			MEM2_WR=0

4. AWC:

PC	→	MEM1_ADDR, ALU2_A	ALU1: ADD
MEM1_DATA ₁₁₋₉	→	RF_A1	MEM1_RD=1

MEM1_DATA ₈₋₆ → RF_A2	RF_WR=1
RF_D1 → ALU1_A	RF_RD=1
RF_D2 → ALU1_B	CMP=0
ALU1_C → ALU4_A	MEM2_RD=0
C → SE1 → ALU4_B	MEM2_WR=0
ALU4_C → RF_D3	
MEM1_DATA ₅₋₃ → RF_A3	
+2 → ALU2_B	
ALU2_C → PC	

5. ACA:
REPLACED CMP=1 IN ADA
6. ACC:
REPLACED CMP=1 IN ADC
7. ACZ:
REPLACED CMP=1 IN ADZ
8. ACW:
REPLACED CMP=1 IN AWC
9. ADI:

PC → MEM1_ADDR , ALU2_A	MEM1_RD=1
MEM1_DATA ₁₁₋₉ → RF_A1	ALU1: ADD
RF_D1 → ALU1_A	RF_RD=1
MEM1_DATA ₅₋₀ → SE6 → ALU1_B	RF_WR=1
MEM1_DATA ₈₋₆ → RF_A3	CMP=0
ALU1_C → RF_D3	MEM2_RD=0
+2 → ALU2_B	MEM2_WR=0
ALU2_C → PC	




10. NDU:

PC → MEM1_ADDR, ALU2_A	MEM1_RD=1
MEM1_DATA ₁₁₋₉ → RF_A1	ALU1: NAND
MEM1_DATA ₈₋₆ → RF_A2	RF_RD=1
RF_D1 → ALU1_A	RF_WR=1
RF_D2 → ALU1_B	CMP=0
ALU1_C → RF_D3	MEM2_RD=0
+2 → ALU2_B	MEM2_WR=0
ALU2_C → PC	

11. NDC:

PC → MEM1_ADDR, ALU2_A	MEM1_RD=1
if (C==1) : NDU	ALU1:NAND
else:	RF_RD=1
+2 → ALU2_B	RF_WR=1
ALU2_C → PC	CMP=0
	MEM2_RD=0
	MEM2_WR=0

12. NDZ:

PC  MEM1_ADDR, ALU2_A if (Z==1) : NDU else: +2  ALU2_B ALU2_C  PC	MEM1_RD=1 ALU:NAND RF_RD=1 RF_WR=1 CMP=0 MEM2_RD=0 MEM2_WR=0
--	--

13. NCU:

REPLACED CMP=1 IN NDU


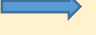
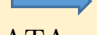



14. NCC:

REPLACED CMP=1 IN NDC








 

 
15. NCZ:

REPLACED CMP=1 IN NDZ




 
 
 


16. LLI:

PC  MEM1_ADDR, ALU2_A +2  ALU2_B ALU2_C  PC MEM1_DATA ₈₋₀  SE9  RF_D3 MEM1_DATA ₁₁₋₉  RF_A3	MEM1_RD=1 RF_RD=0 RF_WR=1 CMP=0 ALU:ADD MEM2_RD=0 MEM2_WR=0
--	---

17. LW:

PC  MEM1_ADDR, ALU2_A +2  ALU2_B ALU2_C  PC MEM1_DATA ₈₋₆  RF_A1 RF_D1  ALU1_A MEM1_DATA ₅₋₀  SE6  ALU1_B ALU1_C  MEM2_ADDR MEM2_DATA  RF_D3 MEM1_DATA  RF_A3	MEM1_RD= 1 ALU1: ADD RF_RD=1 RF_WR= 1 CMP=0 MEM2_RD=1 MEM2_WR=0
---	---

18. SW:

PC  MEM1_ADDR, ALU2_A +2  ALU2_B ALU2_C  PC MEM1_DATA ₅₋₀  SE6  ALU1_B ALU1_C  MEM2_ADDR MEM1_DATA ₁₁₋₉  RF_A2 RF_D2  MEM2_DATA	MEM1_RD=1 ALU1:ADD RF_RD=1 RF_WR=0 MEM2_WR=1 MEM2_RD=0 CMP=0
---	--

19. BEQ:

PC \rightarrow MEM1_ADDR, ALU2_A +2 \rightarrow ALU2_B MEM1_DATA ₁₁₋₉ \rightarrow RF_A1 MEM1_DATA ₈₋₆ \rightarrow RF_A2 RF_D1 \rightarrow ALU1_A RF_D2 \rightarrow ALU1_B ALU2_C \rightarrow ALU3_A MEM1_DATA ₅₋₀ \rightarrow SE6 \rightarrow S-1 \rightarrow ALU3_B if (ALU1_Z==1) : ALU3_C \rightarrow PC else: ALU2_C \rightarrow PC	MEM1_RD=1 ALU3: XOR RF_RD=1 RF_WR=0 MEM2_WR= 0 MEM2_RD=0 CMP=0
--	--

20. BLT :

REPLACED ALU1_Z BY ALU1_C IN BEQ

21. BLE:

REPLACED ALU1_Z BY (ALU1_Z || ALU1_C) IN BEQ

22. JAL:

PC \rightarrow MEM1_ADDR, ALU2_A +2 \rightarrow ALU2_A MEM1_DATA ₁₁₋₉ \rightarrow RF_A3 ALU2_C \rightarrow ALU3_A, RF_A3 MEM1_DATA ₈₋₀ \rightarrow SE9 \rightarrow S-1 \rightarrow ALU3_B ALU3_C \rightarrow PC	MEM1_RD=1 ALU3 : ADD RF_RD= 0 RF_WR= 1 CMP=0 MEM2_RD=0 MEM2_WR=0
--	--

23. JLR:

PC \rightarrow MEM1_ADDR, ALU2_A +2 \rightarrow ALU2_B MEM1_DATA ₁₁₋₉ \rightarrow RF_A3 ALU2_C \rightarrow ALU3_A +0 \rightarrow ALU3_B ALU3_C \rightarrow RF_D3 MEM1_DATA ₈₋₆ \rightarrow RF_A1 RF_D1 \rightarrow PC	MEM1_RD=1 RF_RD=1 RD_WR=1 CMP=0 MEM2_RD=0 MEM2_WR=0 ALU3:ADD
--	--

24. JLI:

PC \rightarrow ALU2_A +2 \rightarrow ALU2_B ALU2_C \rightarrow PC MEM1_DATA ₈₋₀ \rightarrow RF_A1 RF_D1 \rightarrow ALU1_A MEM1_DATA ₈₋₀ \rightarrow SE9 \rightarrow S-1 \rightarrow ALU1_B ALU1_C \rightarrow PC	MEM1_RD=1 RF_RD=1 RF_WR=0 CMP=0 MEM2_RD=0 MEM2_WR=0 ALU1:ADD
---	--

25. LM:

PC → MEM1_ADDR, ALU2_A +2 → ALU2_B ALU2_C → PC MEM1_DATA ₁₁₋₉ → RF_A1 for i: 0 to 7 : [if i==0: if imm(i) ==1: RF_D1 → MEM2_ADDR MEM2_DATA_OUT → RF_D3 111 → RF_D3 RF_D1 → ALU1_A 01 → ALU1_B ALU1_C → RF_D3 MEM1_DATA ₁₁₋₉ → RF_A3] THE ABOVE BLOCK IS REPEATED WITH 111 REPLACED BY 110 AND SO ON TILL i==7	MEM1_RD=1 RF_RD=1 RF_WR=1 ALU1: ADD CMP=0 MEM2_RD=1 MEM2_WR=0S
--	--

26. SM:

PC → MEM1_ADDR, ALU2_A +2 → ALU2_B ALU2_C → PC MEM1_DATA ₁₁₋₉ → RF_A1 for i: 0 to 7: [if i==0: if imm(i)==1: RF_D1 → MEM2_ADDR 111 → RF_A2 RF_D2 → MEM2_DATA_IN RF_D1 → ALU1_A 01 → ALU1_B ALU1_C → RF_D3 MEM1_DATA ₁₁₋₉ → RF_A3] REPEATED SAME AS ABOVE TILL i==7	MEM1_RD=1 CMP=0 RF_WR=1 RF_RD=1 MEM2_WR=1 MEM2_RD=0 ALU1: ADD
--	---

Control Variables:

Instruction	Opcode	PCWR	MEM1RD	MUX9	RFRD	RFWR	MUX1	MUX2	MUX3	MUX4	MUX5	MUX7	S11	S12	CMP	CIN	ZIN	MUX6	MUX10	CV	EN	MEM2RD	MEM2WR	MUX8	
ADA	0001	1	1	0	1	1	1	0	01	1	11	01	0	0	0	0	0	1	10 00	11		0	0	0	
ADC	0001	1	1	0	1	1	1	0	01	1	11	01	0	0	0	1	0	1	10 00	11		0	0	0	
ADZ	0001	1	1	0	1	1	1	0	01	1	11	01	0	0	0	0	1	1	10 00	11		0	0	0	
AWC	0001	1	1	0	1	1	1	0	01	1	11	01	0	0	0	1	1	1	11 00	11		0	0	0	
ACA	0001	1	1	0	1	1	1	0	01	1	11	01	0	0	1	0	0	1	11 00	11		0	0	0	
ACC	0001	1	1	0	1	1	1	0	01	1	11	01	0	0	1	1	0	1	11 00	11		0	0	0	
ACZ	0001	1	1	0	1	1	1	0	01	1	11	01	0	0	1	0	1	1	11 00	11		0	0	0	
ACW	0001	1	1	0	1	1	1	0	01	1	11	01	0	0	1	1	1	1	11 00	11		0	0	0	
ADI	0000	1	1	0	1	1	1	X	10	1	10	01	0	0	0	X	X	1	10 00	11		0	0	0	
NDU	0010	1	1	0	1	1	1	0	01	1	11	01	0	0	0	0	0	1	10 01	01		0	0	0	
NDC	0010	1	1	0	1	1	1	0	01	1	11	01	0	0	0	1	0	1	10 01	01		0	0	0	
NDZ	0010	1	1	0	1	1	1	0	01	1	11	01	0	0	0	0	1	1	10 01	01		0	0	0	
NCU	0010	1	1	0	1	1	1	0	01	1	11	01	0	0	1	0	0	1	10 01	01		0	0	0	
NCC	0010	1	1	0	1	1	1	0	01	1	11	01	0	0	0	1	1	0	1	10 01	01		0	0	0
NCZ	0010	1	1	0	1	1	1	0	01	1	11	01	0	0	1	0	1	1	10 01	01		0	0	0	
LLI	0011	1	1	0	0	1	X	X	11	0	00	01	0	0	0	X	X	1	10 00	00		0	0	0	
LW	0100	1	1	0	1	1	0	X	11	1	10	01	0	0	0	X	X	1	X 00	00		1	1	1	
SW	0101	1	1	0	1	1	0	1	00	1	11	01	0	0	0	0	X	X	1	01 00	00		1	1	0
LM	0110																		01 00	00					
SM	0111																								
BEQ	1000	1	1		1	0	1	0	X	1	11	11	0	0	0	X	X	1	X 00	00		0	0	X	
BLT	1001	1	1		1	0	1	0	X	1	11	11	0	0	0	X	X	1	X 00	00		0	0	X	
BLE	1001	1	1		1	0	1	0	X	1	11	11	0	0	0	X	X	1	X 00	00		0	0	X	
JAL	1100	1	1	1	0	1	X	X	11	X	X	10	0	0	0	X	X	1	01 X	00		0	0	0	
JLR	1101	1	1	1	1	1	0	X	11	X	X	01	0	0	0	X	X	1	01 X	00		0	0	0	
JRI	1111	1	1	1	X	0	1	X	X	1	01	01	0	0	0	0	X	X	1	X X	00		0	0	X

Entities:

1. ALU1, ALU2, ALU3: ALUs meant for arithmetic and logical operations. There is also an additional ALU4 inside EX stage, however it's code is not there in the entities folder exclusively.
2. Branch_Jump_control: To control MUX9's output when branch or jump instructions happen.
3. Data_memory: Memory block 2, used to store data.
4. Instruction_memory: Memory block 1, used to store instructions.
5. data_hazard_1, data_hazard_2, data_hazard_3: These blocks check for data dependencies and do the requisite data forwarding.
6. Pipe_Register_control: To control the flow of information through the pipeline registers and stall the stages, as and when required.
7. Register_file: Contains 16-bit registers from R0-R7.
8. SE1: Sign extender for 1-bit data.
9. SE6: Sign extender for 6-bit data.
10. SE9: Sign extender for 9-bit data.
11. Shifter: 1-bit left shifter.
12. Stages: Contains the code required for each stage. Note that we do not need to design an entity for WB stage explicitly.

[GITHUB Link](#)